


## 7. MICROSTRIP POWER DIVIDER

**Aim:** 1. To design and simulation of a T-junction power divider for equal and unequal power divisions.

2. To determine the scattering parameters of T-junction power divider.

**Equipment required:** HFSS Circuit Design


<b>Specifications:</b>	Characteristic impedance	$Z_0 =$
	Operating frequency	$f =$
	Substrate thickness	$H =$
	Metal thickness	$T =$
	Dielectric constant	$\epsilon_r =$
	Loss tangent	$L =$

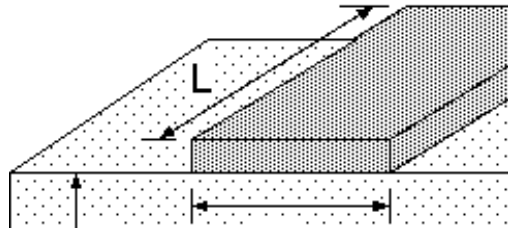

**Figure (1)**

**Theory:** The power divider is generally designed using microstrip lines as shown in figure 2 and can be made with any number of ports with equal or unequal power divisions.

**Figure (2)**

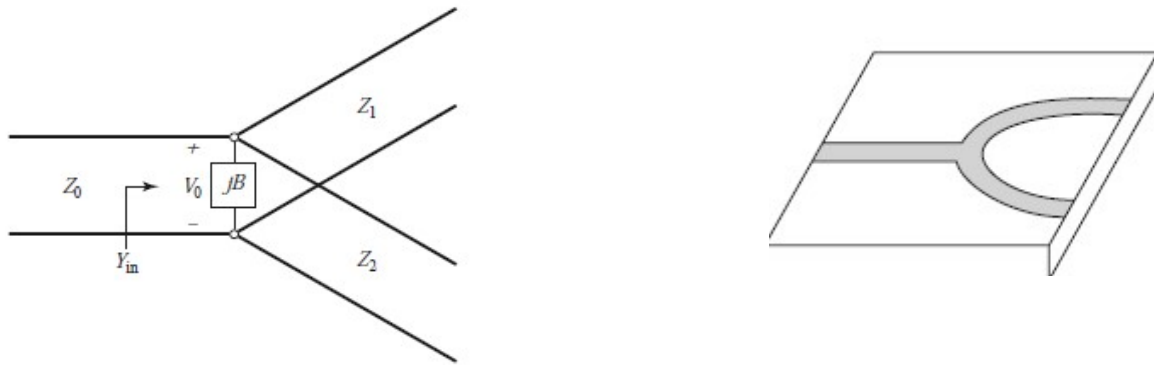

$$Y_{\text{in}} = jB + \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}.$$

**Design Equations: (from 2:1 equal power division)**

$$P_{\text{in}} = \frac{1}{2} \frac{V_0^2}{Z_0},$$


while the output powers are

$$P_1 = \frac{1}{2} \frac{V_0^2}{Z_1} = \frac{1}{3} P_{\text{in}},$$

$$P_2 = \frac{1}{2} \frac{V_0^2}{Z_2} = \frac{2}{3} P_{\text{in}}.$$

## Design of Microstrip Power divider in HFSS Circuit Design:

*Note: Follow the procedure steps in 7 experiment to set the layout.*

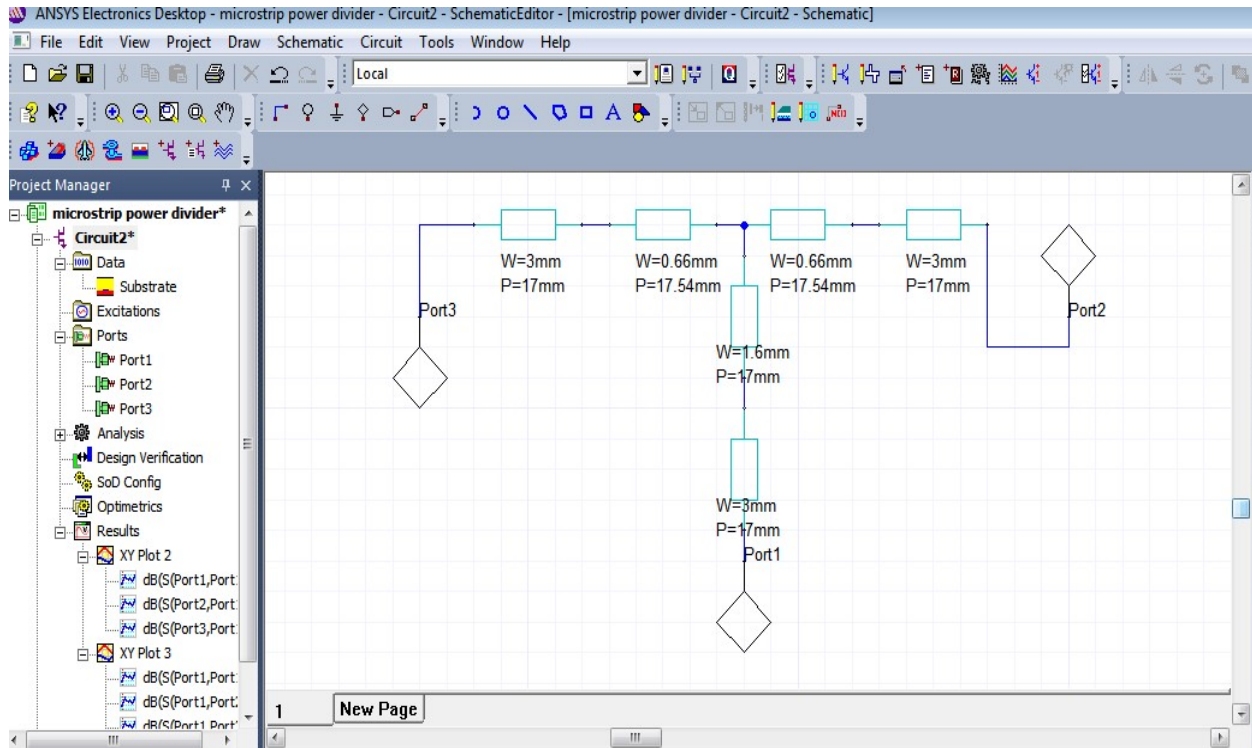

**Fig. 1: Power divider layout in HFSS**

**Sample Observations:** For equal power division, sample results of a power divider shown below

$$Z_0 = 50 \, \Omega, f = 2.4 \, \text{GHz}, H = 1.6 \, \text{mm}, T = 0.036 \, \text{mm}, \epsilon_r = 4.4, L = 0.001$$

## Model graph:

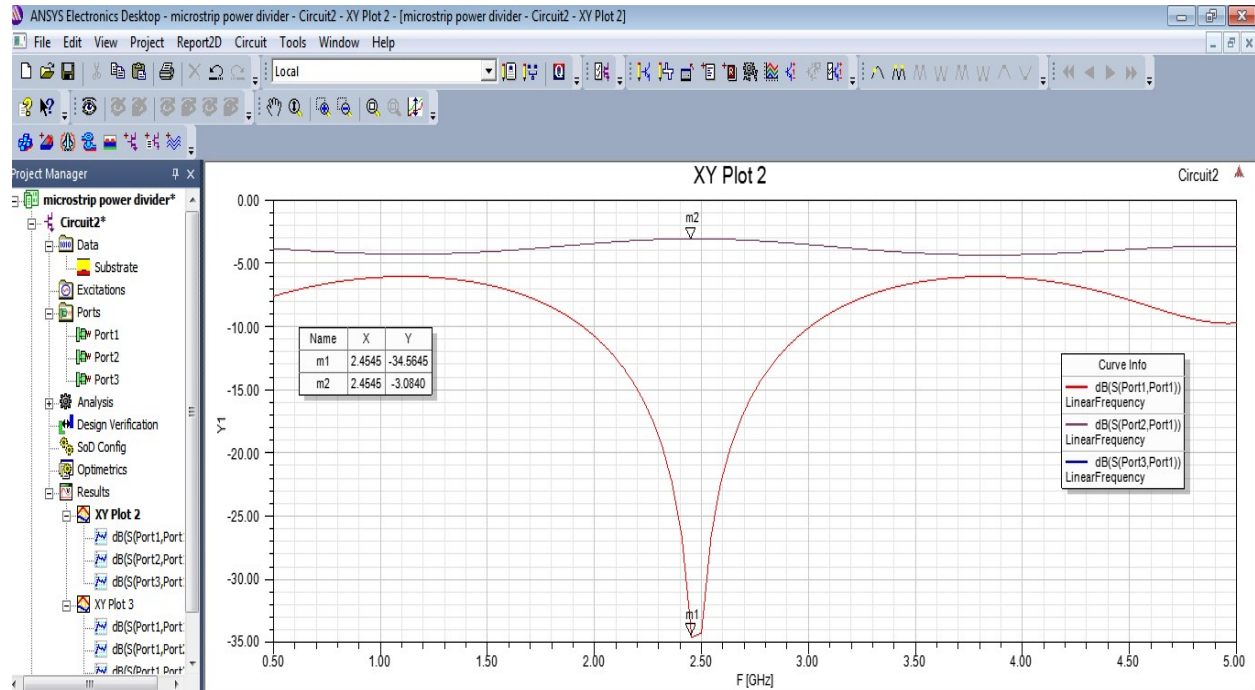


Figure 2: S-parameters of Power divider

## Practical Observations:

Frequency	$S_{11}$	$S_{21}$	$S_{31}$	$S_{32}$

## Conclusions:

The power is equally split in the both arms